
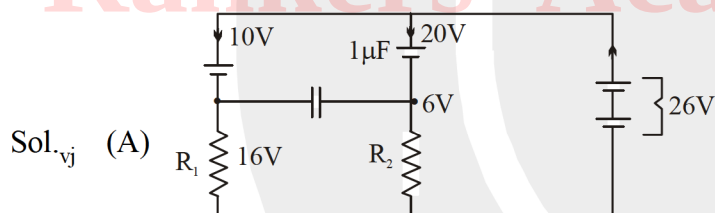


HINTS AND SOLUTIONS

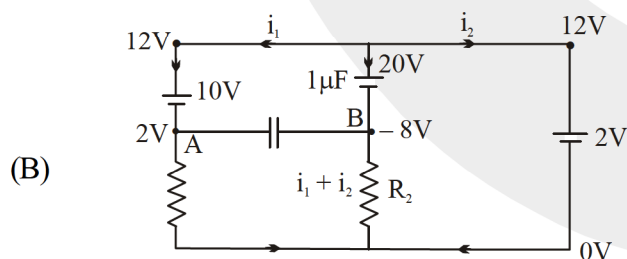
- Q.1 A
Q.2 C
Q.3 B
Q.4 C
Q.5 A
Q.6 B
Q.7 B
Q.8 A
Q.9 A
Q.10 B
Q.11 B
Q.12 A
Q.13 C
Q.14 C
Q.15 D
Q.16 B
Q.17 ABCD
Q.18 A
Q.19 A
Q.20 [Ans. (A) P,Q,S ; (B) P,Q,R,S ; (C) P,Q,S ; (D) P,Q,R,S]




P.D. across capacitance is $10 \mu\text{C}$
By analysing circuit P, Q, S is correct



By analysing P, R, S is correct

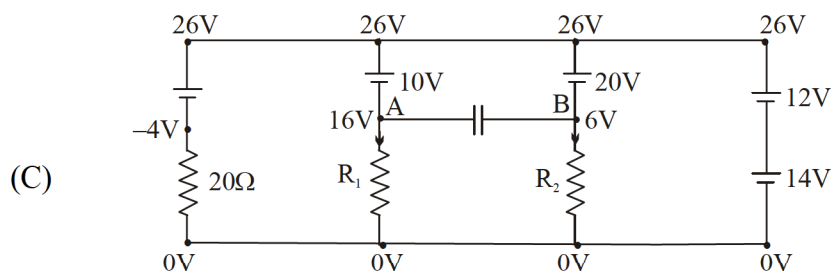

By analysis (P), (Q), (S)

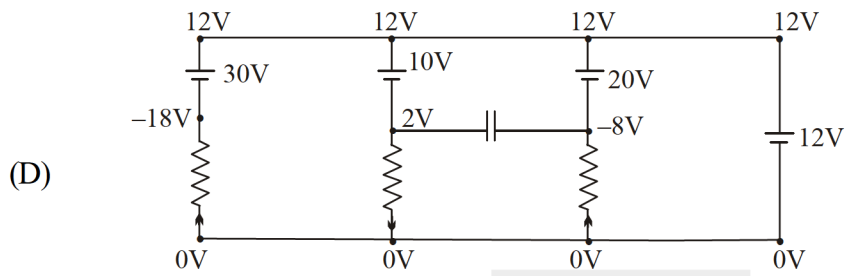

By analysis.

Q.21 [Ans. 4 mF]

Q.22 Ans. 1Ω

Rankers Academy JEE